

Mark Lucernas
Tamara Sagakova

Unit 4 Lab (Group Lab Assignment)

Time spent on the lab:

10 hours

Table 1:

Hexadecimal Digit	Inputs				Outputs							(in hex)
	D ₃	D ₂	D ₁	D ₀	S _g	S _f	S _e	S _d	S _c	S _b	S _a	
0	0	0	0	0	1	0	0	0	0	0	0	40
1	0	0	0	1	1	1	1	1	0	0	1	79
2	0	0	1	0	0	1	0	0	1	0	0	24
3	0	0	1	1	0	1	1	0	0	0	0	30
4	0	1	0	0	0	0	1	1	0	0	1	19
5	0	1	0	1	0	0	1	0	0	1	0	12
6	0	1	1	0	0	0	0	0	0	1	0	2
7	0	1	1	1	1	1	1	1	0	0	0	78
8	1	0	0	0	0	0	0	0	0	0	0	0
9	1	0	0	1	0	0	1	1	0	0	0	18
A	1	0	1	0	0	0	0	1	0	0	0	8
B	1	0	1	1	0	0	0	0	0	1	1	3
C	1	1	0	0	0	1	0	0	1	1	1	27
D	1	1	0	1	0	1	0	0	0	0	1	21
E	1	1	1	0	0	0	0	0	1	1	0	6
F	1	1	1	1	0	0	0	1	1	1	0	E

Table 1. Truth table for 7-segment display decoder

Equations:

$$S_g = \overline{D_3} \overline{D_2} \overline{D_1} + \overline{D_3} D_2 D_1 D_0$$

$$S_f = \overline{D_3} \overline{D_2} D_0 + \overline{D_3} D_1 D_0 + \overline{D_3} \overline{D_2} D_1 + D_3 D_2 \overline{D_1}$$


$$S_e = \overline{D_2} \overline{D_1} D_0 + \overline{D_3} D_0 + \overline{D_3} D_2 \overline{D_1}$$

$$S_d = \overline{D_2} \overline{D_1} D_0 + \overline{D_3} D_2 \overline{D_1} \overline{D_0} + D_2 D_1 D_0 + D_3 \overline{D_2} D_1 \overline{D_0}$$

$$S_c = \overline{D_3} \overline{D_2} D_1 \overline{D_0} + D_3 D_2 \overline{D_0} + D_3 D_2 D_1$$

$$S_b = \overline{D_3} D_2 \overline{D_1} D_0 + D_2 D_1 \overline{D_0} + D_3 D_1 D_0 + D_3 D_2 (D_1 + \overline{D_0})$$

 
$$S_a = \overline{D_3} \overline{D_2} \overline{D_1} D_0 + D_2 \overline{D_1} \overline{D_0} + D_3 D_2 \overline{D_1} + D_3 \overline{D_2} D_1 D_0$$



Description:

The design method we used is of a combinational logic design. It takes in 4 inputs and has 7 outputs. We used a combinational logic design because it does not require to be synchronous or asynchronous. It can be used in conjunction with memory or register and some flip flop circuits to turn into a sequential circuit.


Stimulation:

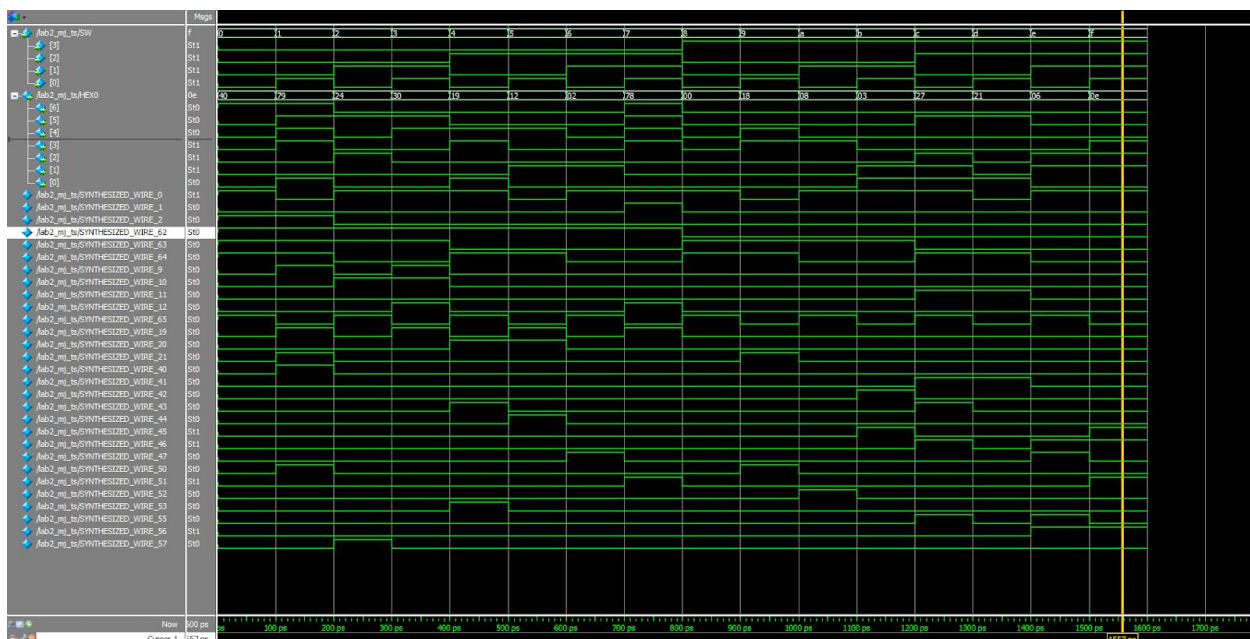


The diagram illustrates a 6-bit adder circuit. It consists of four 1-bit full adders (inst1, inst2, inst3, inst4) and a 6-bit carry-in (CIN). The circuit uses a hierarchy of AND, OR, and NOT gates to compute the sum of two 6-bit numbers. The final output is a 6-bit hexadecimal value (HEX[5:0]).

Computer drawn schematic:


↓ Part 1

 

↓ Part 2:

 

↓ Part 3

 

↓ Part 4

