

Mark Lucernas  
Tamara Sagakova

### Unit 3 Lab (Group Lab Assignment)

Time spent on the lab:

7 hours


Purpose of the lab:

This lab is for designing simulation of Full Adder in ModelSim. The purpose of the Full Adder is to add two 1 bit binary digits together with a carry ( $C_{in}$ ) to make a single binary addition that produces two outputs: sum ( $S$ ) and a carry ( $C_{out}$ ). Multiple Full Adders is used to add multiple binary digits. Simple Full Adder equation: The output Sum ( $S$ ) is given by inputs  $A \oplus B \oplus C_{in}$ , and output carry ( $C_{out}$ ) is given by the inputs  $AB + C_{in}(A \oplus B)$ .

Truth table:

Inputs			Outputs	
$C_{in}$	$B$	$A$	$C_{out}$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Schematic:

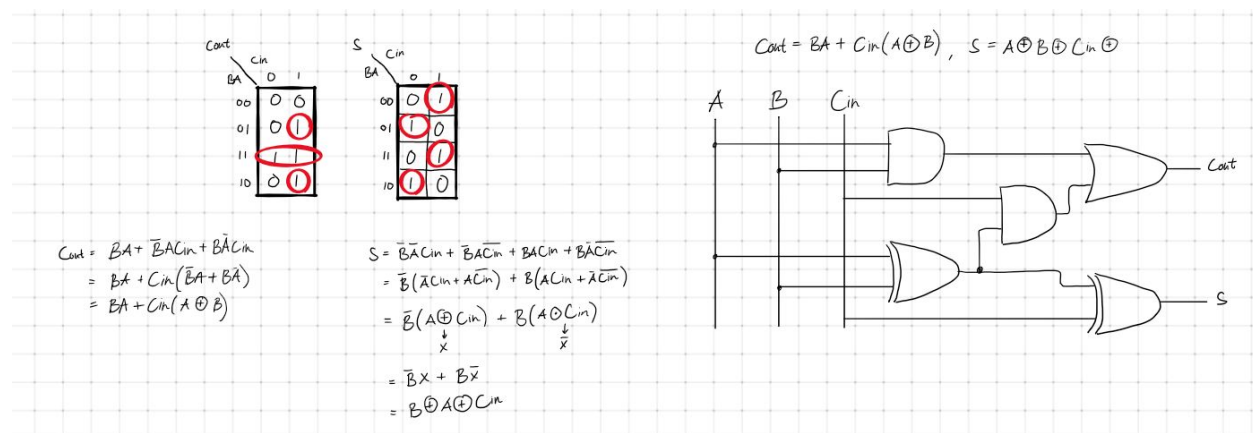

Stimulation of the full adder:

