
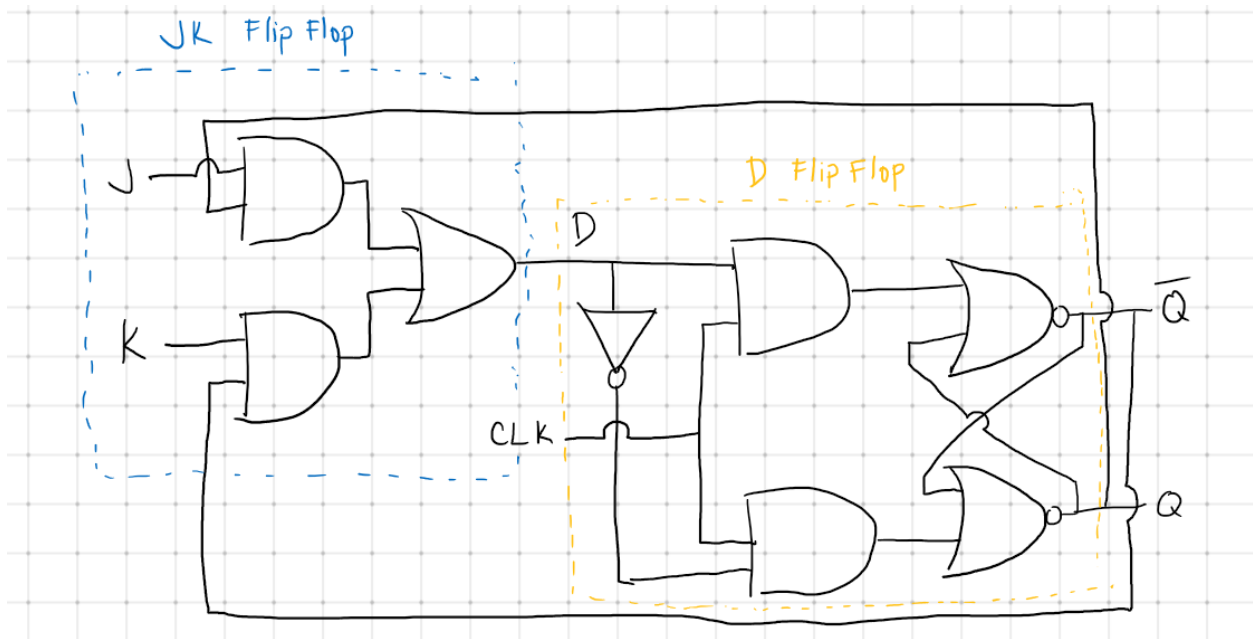


3.10a

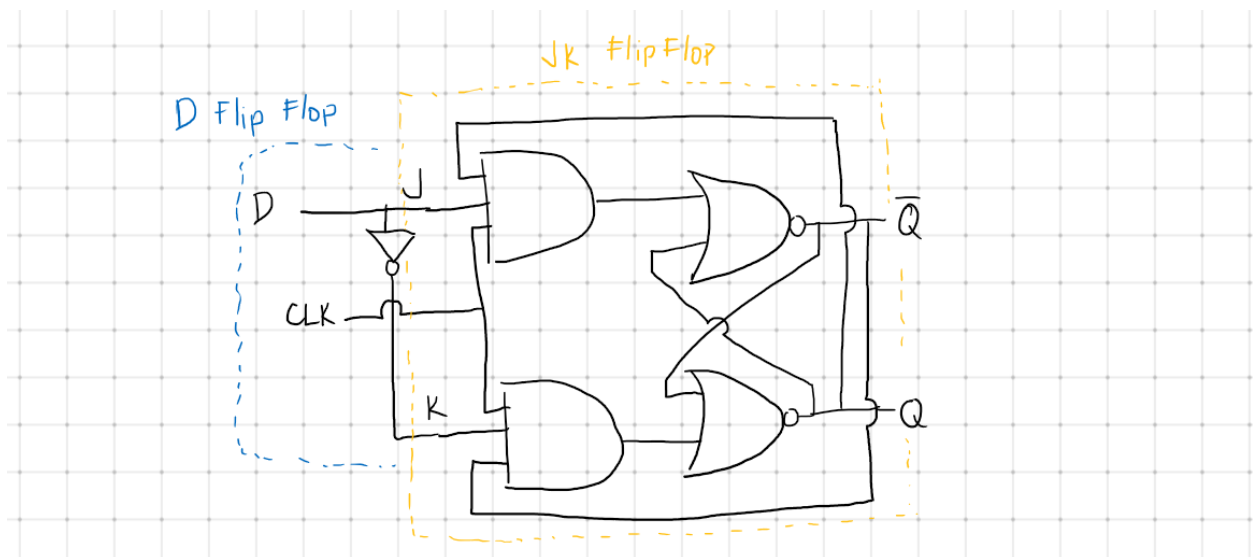

3.10b



3.20

FSM States = $5^4 = 625$. Requires 2^{10} or 10 bits to represent all 625 states.

3.22

This Moore FSM asserts the output Q every clock cycle if A is TRUE followed by B being TRUE.

State Encoding Table

State	Encoding $s_{1,0}$
s_0	00
s_1	01
s_2	10

State Transition Table with Binary Encodings

Current State		Inputs		Next State	
s_1	s_0	a	b	s'_1	s'_0
0	0	0	X	0	0
0	0	1	X	0	1
0	1	X	0	0	0
0	1	X	1	1	0
1	0	X	X	0	0

Output Table with Binary Encodings

Current State		Output
s_1	s_0	Q
0	0	0
0	1	0
1	0	1

